

CS 340

Building Blocks 0b01

clicker.cs.illinois.edu

Q1

~Code~
340




Updates

1. MP 0 - Setup due TOMORROW.
2. MP 1 - debugger due TODAY.
3. MP 2 - Linked-List in C due next Tuesday
4. If you added late, let us know ASAP for possible extensions
5. HW 1 Due Wednesday 11:59pm
 - a. No debugger on PL

Review

```
22 void setString(char **str) {  
23     *str="Hello";  
24 }  
  
25  
26 int main() {  
27     char *s = "World";  
28     setString(&s);  
29     printf("%s", s);  
30     return 0;  
31 }
```

'0' = 48 '0' = 0 ← end of c-string

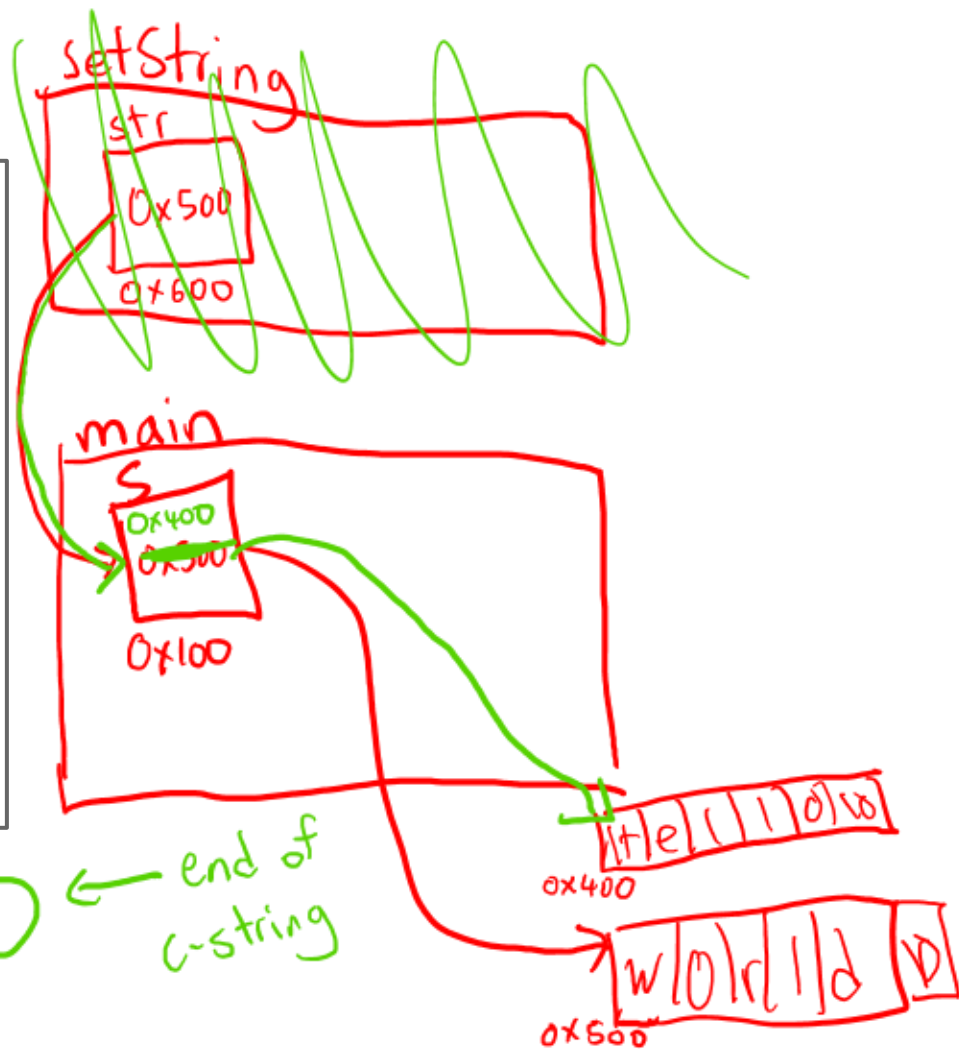

Building Blocks 0b01


LG: Help you understand how logic is built using hardware

Mental Models Developed

How a computer works at a physical level

Agenda

1. Circuit and Gate Basics
2. Binary

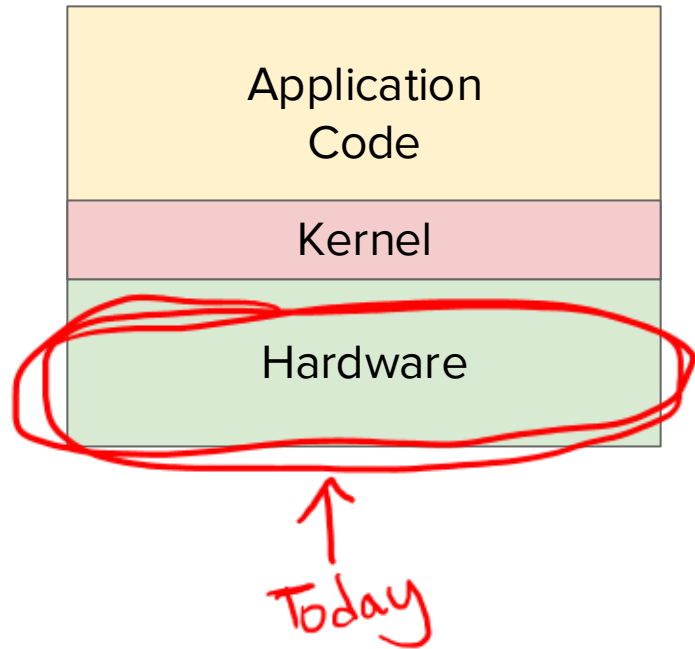

Not a
physics
class

Circuit and Gate Basics

Idea 1: Nodes Hold Voltage

Node - example - wire - ends of a battery

Voltage - a state - electric potential energy

Current - movement - charge moving to equalize voltage between nodes


Idea 2: Two Important Nodes

Power - V , high, 1 pushes charge away

Ground - G , low, 0 pulls charge towards it

if directly connected it will short circuit
* too much current!

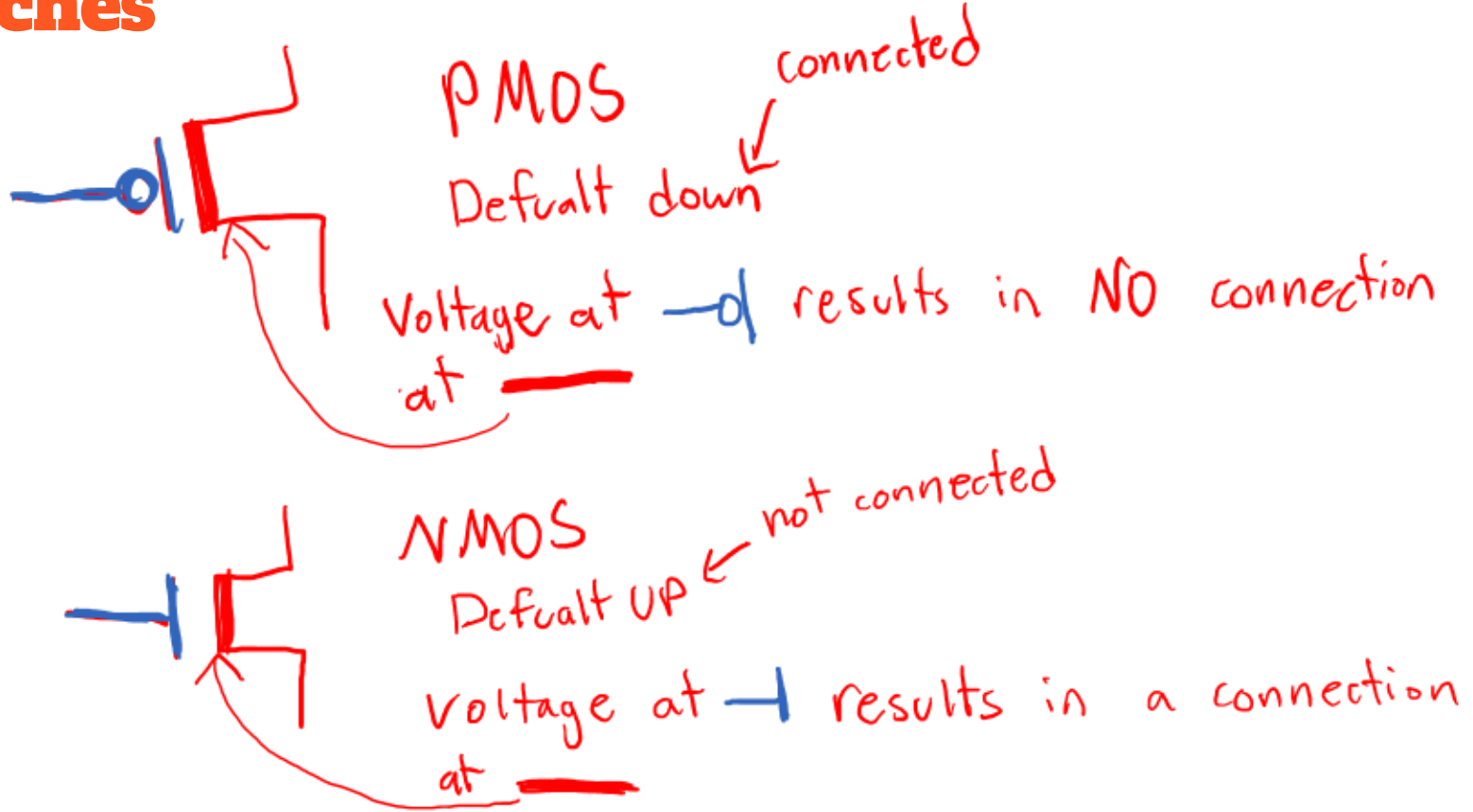Idea 3: Transistors are voltage-controlled switches



Big Ideas


Nodes hold voltage.

Current flows from high to low voltage to equalize voltage.

Power and ground are two important nodes needed.

Transistors are voltage-controlled switches.


Example Circuit

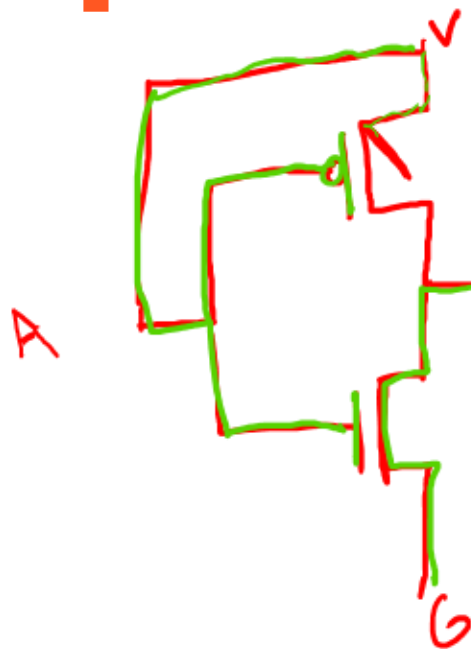

This results
in C having
0 volts

0V

What voltage does the node C hold?

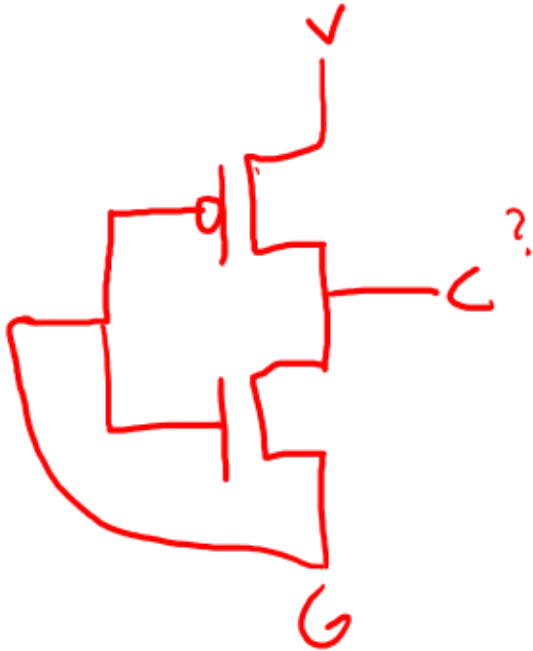

- a) high
- b) low
- c) undetermined

clicker.cs.illinois.edu

Q2

~Code~
340




Gates

Take input(s) voltage and result in... high or low voltage at the output


Gates use... transistors with input voltage to control output voltage

Gates can be used to... implement logic –
AND, OR, NOT, NAND, NOR, XOR

Example Gate

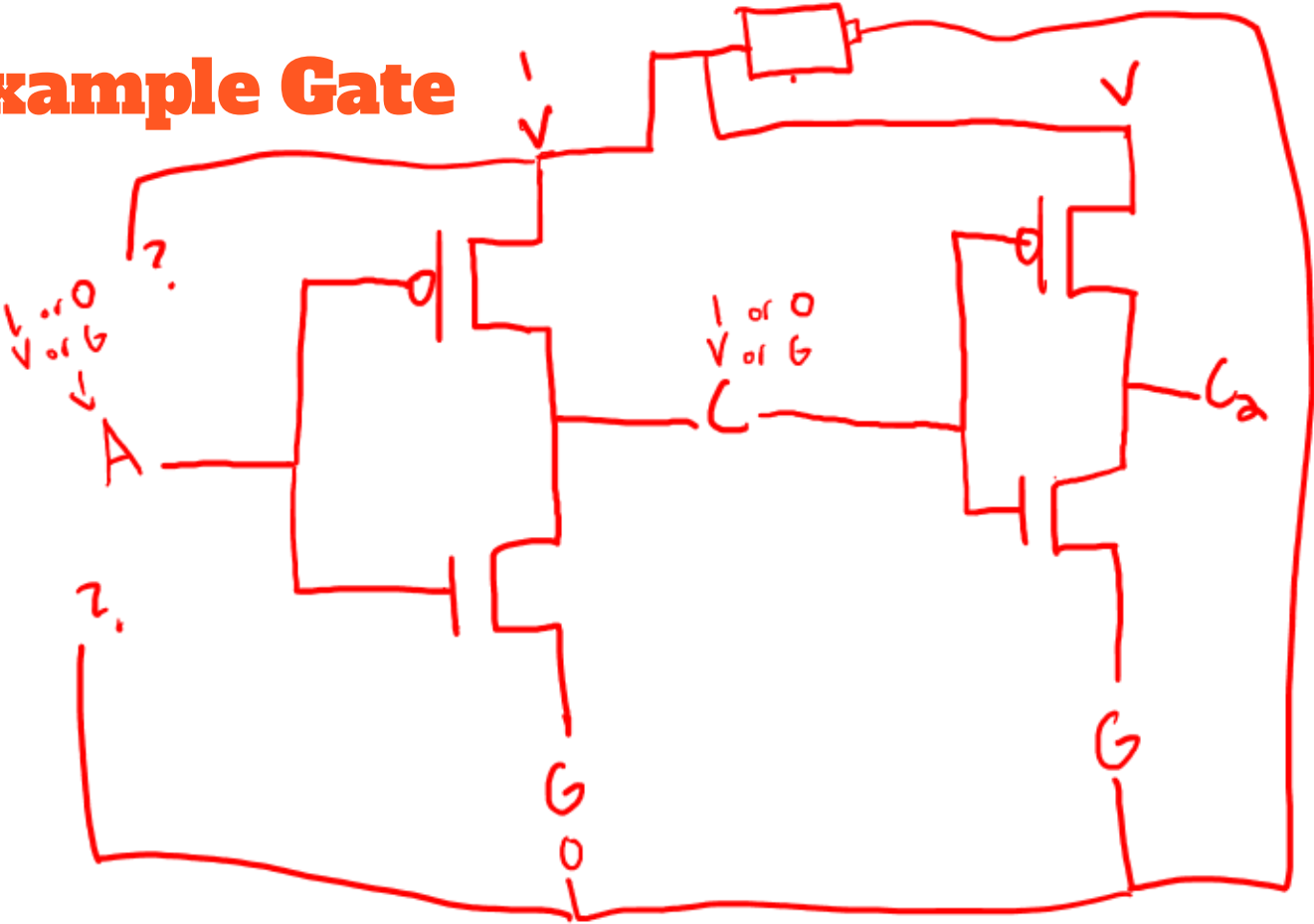

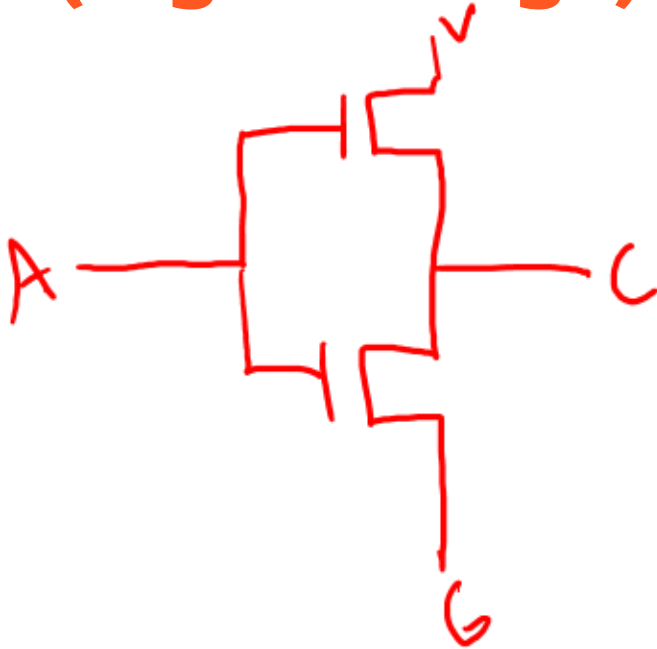What is the voltage at C if A is 1 (high voltage)



clicker.cs.illinois.edu


Q3

~Code~
340




- a) high
- b) low
- c) short circuit

Example Gate

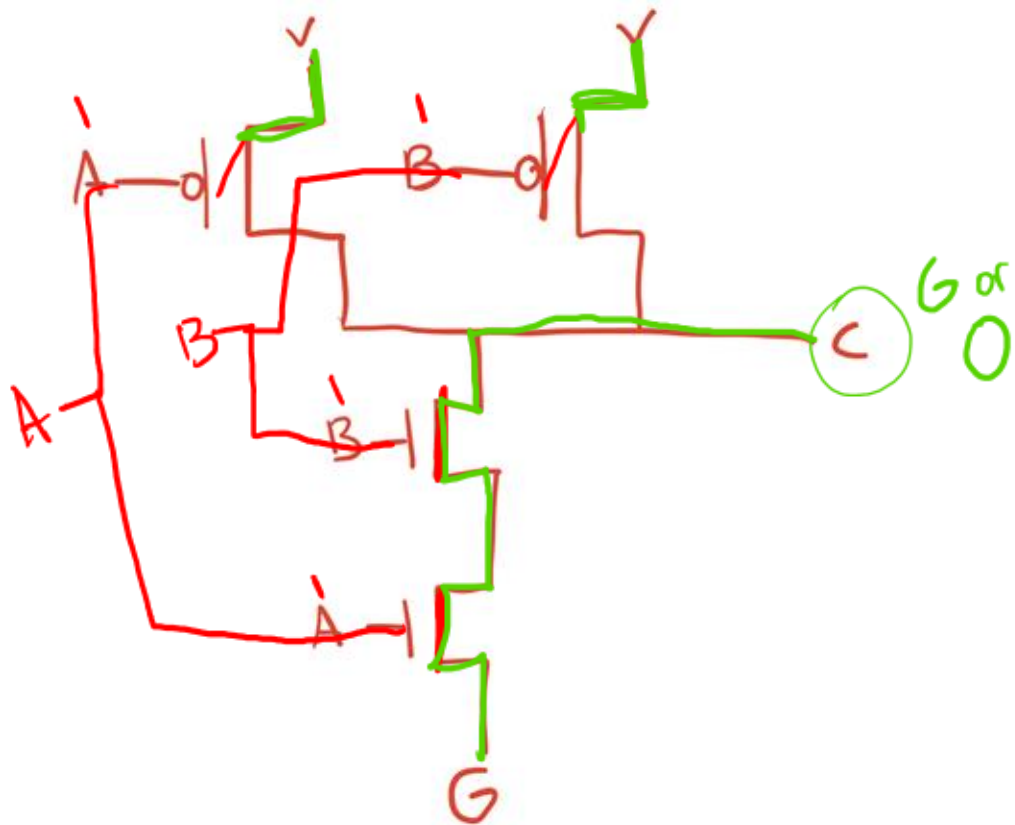

A	B	C
1	1	0
0	0	1
0	1	1
1	0	1

Example Gate

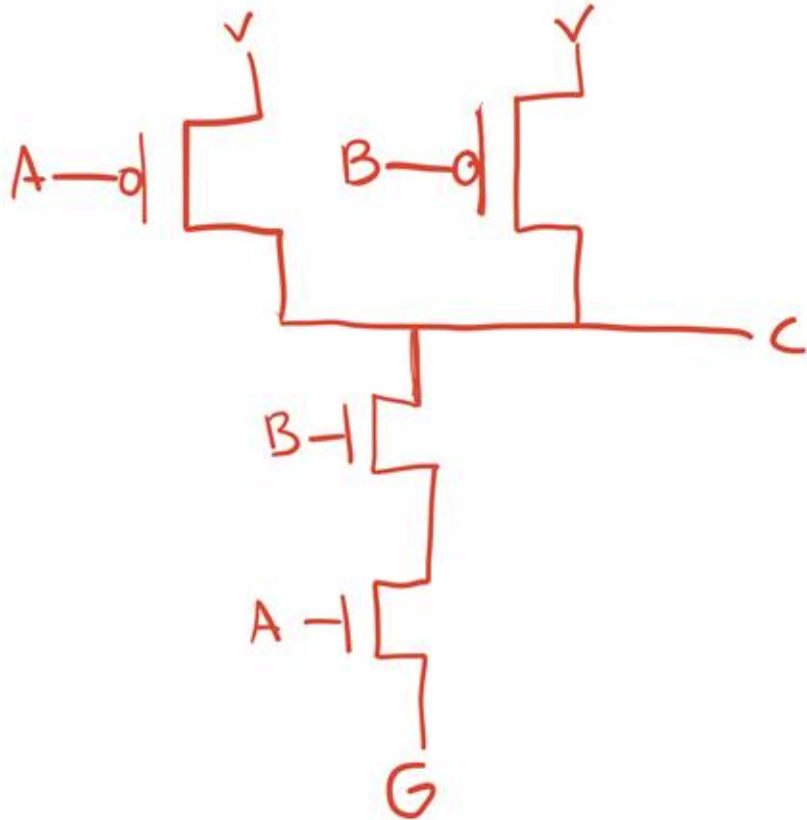

clicker.cs.illinois.edu

Q4

~Code~
340




if A is 0 and B is 0?
what is C ?

a) 0

b) 1

Example Gate

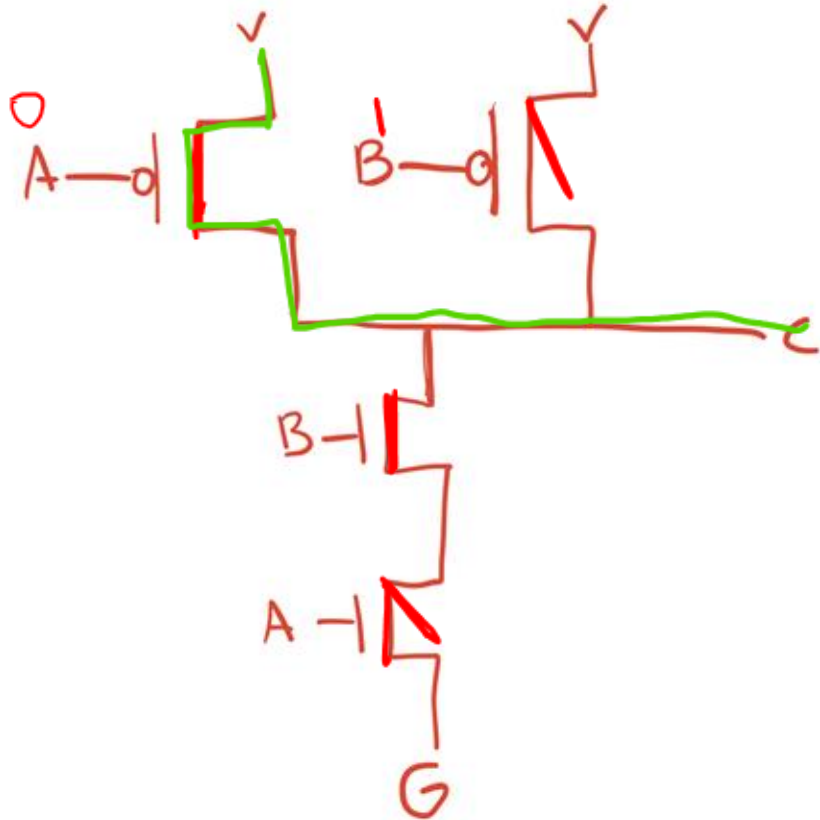

clicker.cs.illinois.edu

Q5

~Code~
340




if A is 0 and B is 1
what is c?

a) 1

b) 0

Example Gate

what is the gate?

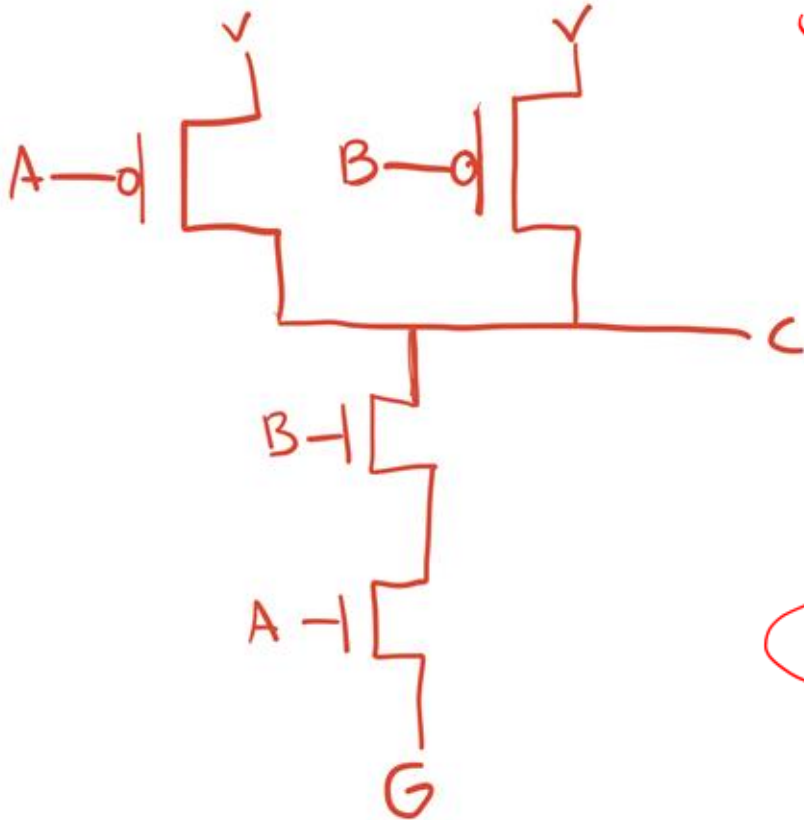

- a) XOR
- b) NOR
- c) AND
- d) NAND


clicker.cs.illinois.edu

Q6

~Code~
340



Example Gate

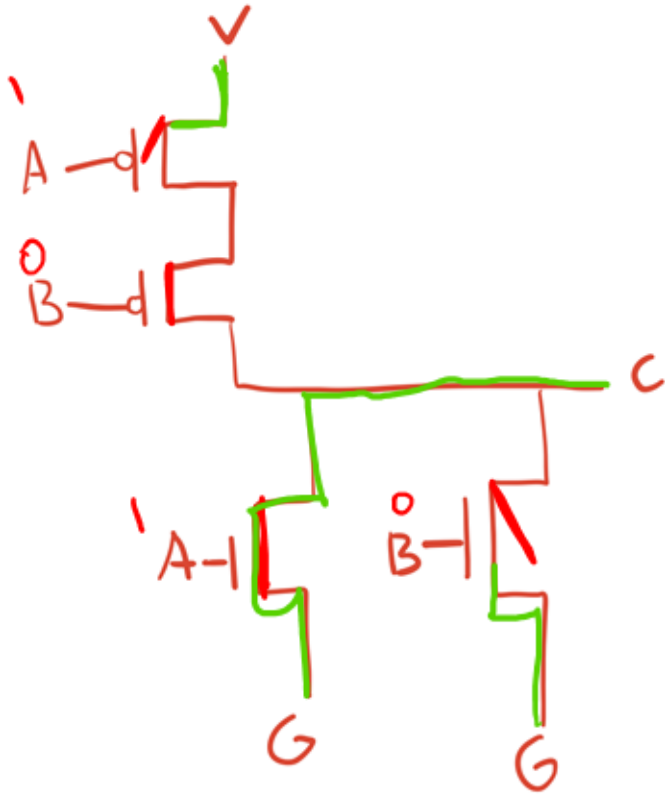

A	B	C
1	0	0
0	1	0
0	0	1
1	1	0

clicker.cs.illinois.edu

Q7

~Code~
340




NOR

if A is 1 and
B is 0 what
is C?

all
b) 0

Example Gate

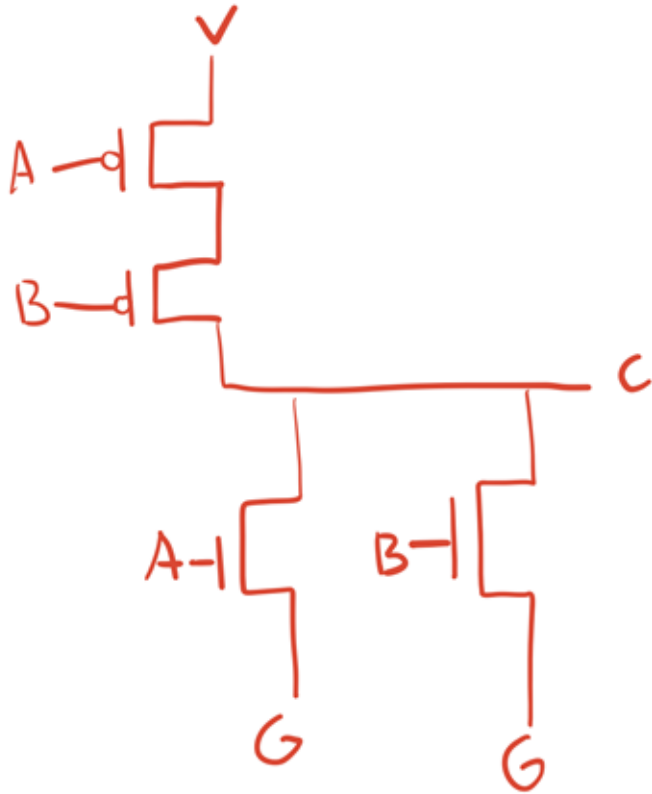

~~is~~
what is
the gate?

NOR

clicker.cs.illinois.edu

Q8

~Code~
340



Implications

electricity \rightarrow logic gates \rightarrow logic, math, selection

we can create any truth table logic
-AND, NAND, XOR ect

Gates work with $\uparrow \downarrow$ voltage 1, 0
so we use binary!

The Binary Number System

Number Systems

We have infinite amounts but finite digits.
To represent big numbers we combine digits.

$$\begin{array}{ccc} 5 & 7 & 8 \\ \uparrow & \uparrow & \uparrow \\ 10^2 & 10^1 & 10^0 \\ 500 + 70 + 8 \end{array}$$

Base-2 Number System

represent numbers using two digits, 0 and 1

$$\textcircled{1} = \textcircled{0b01}$$

↑
indicates
base-2


$$\begin{array}{c} \textcircled{1} \textcircled{1} \\ \textcircled{1} \end{array} = 0b11$$

↑ represents the amount of apples
in base-2


Going from Binary to Decimal

$$\begin{array}{cccccc} 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\ & \downarrow & & \downarrow & & \downarrow & \\ & 32 & + & 4 & + & 1 & = 37 \end{array}$$

Powers of 2 Practice....

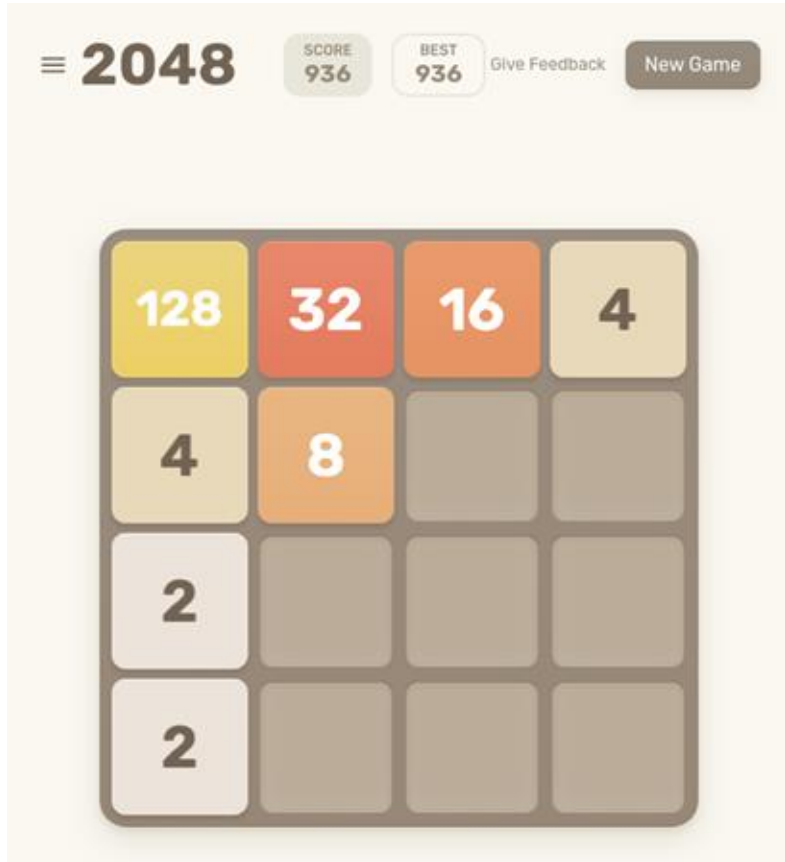

What is 0b10111 in Decimal?

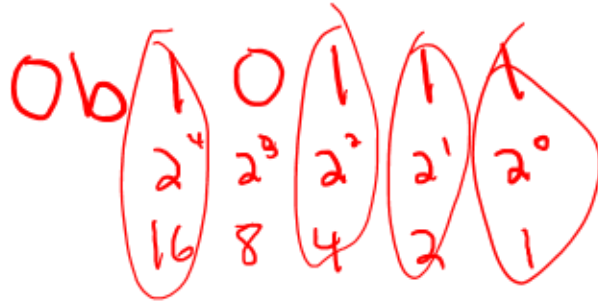

$$16 + 4 + 2 + 1 = 23$$


clicker.cs.illinois.edu

Q9

~Code~
340



Going from Decimal to Binary

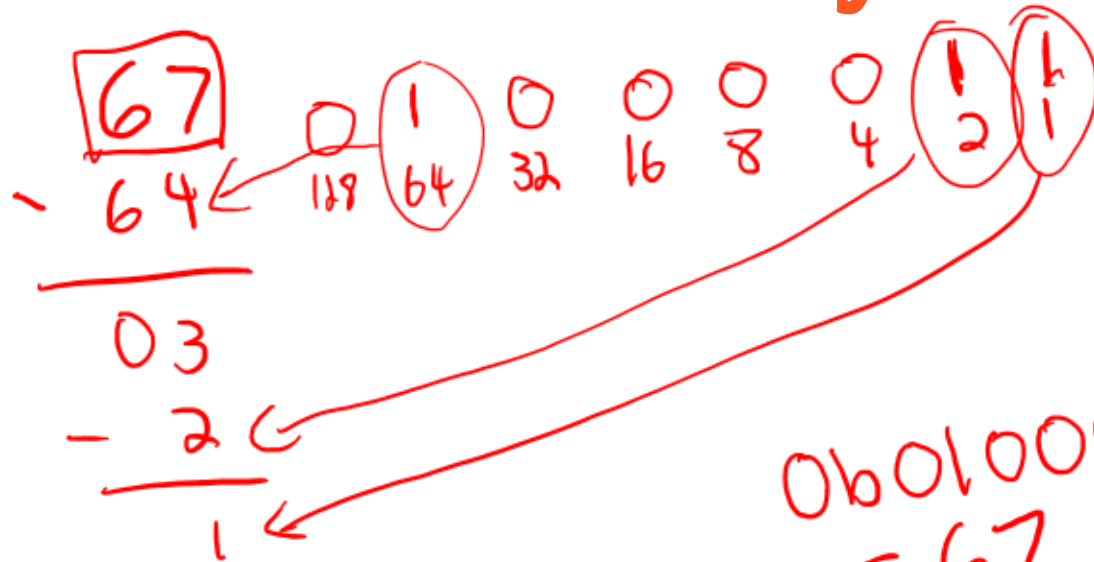

What is 14 in binary?

16	8	4	2	1
0	1	1	1	0

$$\begin{array}{r} 14 \\ - 8 \\ \hline 6 \\ - 4 \\ \hline 2 \end{array}$$

01110

clicker.cs.illinois.edu

Q10

~Code~
340



Counting in Binary

001 \rightarrow 1

010 \rightarrow 2

011 \rightarrow 3

100 \rightarrow 4

101 \rightarrow 5

110 \rightarrow 6

111 \rightarrow 7

What is 0b0001 + 0b1001 in decimal?

0b1010
8 2 = 10

clicker.cs.illinois.edu

Q11

~Code~
340



What is 0b11111 in Decimal?

16 8 4 2 1

$$32 - 1 = 31$$

clicker.cs.illinois.edu

Q12

~Code~
340



Addition in Binary

$$\begin{array}{r} 11011 \\ + 11001 \\ \hline 110100 \end{array}$$

**Bits take up space in hardware.
How many bits of space would I
need to fully represent the
result of $0b11011 + 0b11001$?**

5 4 3 2 1

- a) 4
 - b) 5
 - c) 6
- ← extra bit

clicker.cs.illinois.edu

Q13

~Code~
340



Subtraction in Binary

$$\begin{array}{r} 011 \\ \cancel{1000}1 \\ - 01111 \\ \hline 00010 \end{array}$$

$$\begin{array}{r} 999 \\ \cancel{1000}01 \\ 00011 \\ \hline 99990 \end{array}$$

Big Takeaways

Computers are built with gates.

Gates work with high or low voltages.

We use binary to work with high or low
(1) (0)

What do these bits mean?

~~00~~0100101

a) 37

b) part of a computer instruction -

c) Part of a internet packet

d) can't tell, need context

clicker.cs.illinois.edu

Q14

~Code~
340



What is 100 in Decimal?

↑
Not
binary
there is
no Ob
header

100

clicker.cs.illinois.edu

Q15

~Code~
340

